


# LAB IVERILOG 3

MSI

Version: nOV 28<sup>th</sup> 2016

Lưu ý là test bench và mã module được viết trong cùng một file .v

## I. Comparator

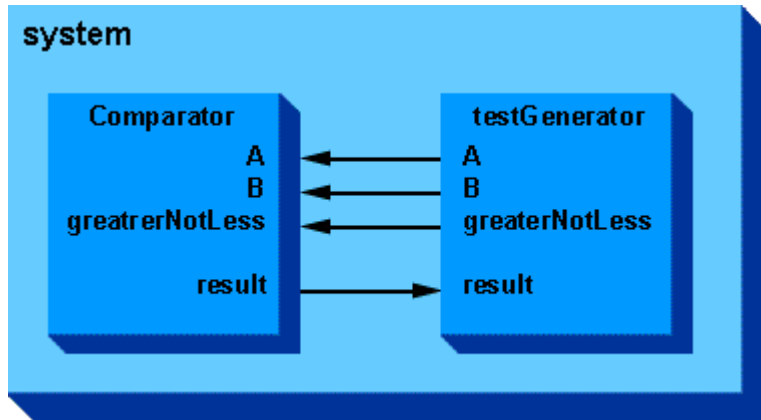

```
module system;
    /* This is a test fixture for
    testing a comparator */

    wire greaterNotLess;
    // sense of comparison
    wire [15:0] A, B;
    // comparand values - 16 bit
    wire result;
    // comparison result

    // Module instances
    comparator #(16, 2) comp
    (result, A, B, greaterNotLess);
    testGenerator tg (A, B,
    greaterNotLess, result);

endmodule

module comparator (result, A, B,
greaterNotLess);
    parameter width = 8;
    parameter delay = 1;
    input [width-1:0] A, B;
    // comparands
    input greaterNotLess;
    // 1 - greater, 0 - less than
    output result;
    // 1 if true, 0 if false

    assign #delay result =
    greaterNotLess ? (A > B) : (A <
    B);
```

```

endmodule

module testGenerator (A, B,
greaterNotLess, result);
    output [15:0] A, B;
    output greaterNotLess;
    input result;
    parameter del = 5;

    reg [15:0] A, B;
    reg greaterNotLess;



    initial begin
// produce test data, check
results
        A = 16'h1234;
        B = 16'b0001001000110100;
        greaterNotLess = 0;
    #del
        check(0);
        B = 0;
        greaterNotLess = 1;
    #del
        check(1);
        A = 1;
        greaterNotLess = 0;
    #del
        check(0);
        $finish;
    end

    task check;
        input shouldBe;
        begin
            if (result !=
shouldBe)
                $display("Error!
%d %s %d, result = %b", A,
greaterNotLess?">":"<",
                                B,
result);
        end
    endtask
endmodule

```

Biên dịch đoạn code trên và quan sát kết quả.

## II. Shift Reg with Counter

 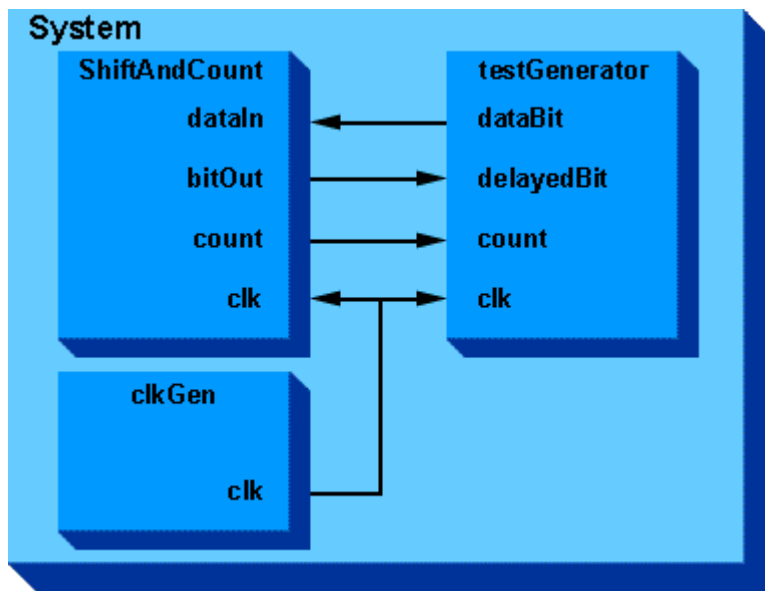

```

module system;
    /* This is a test fixture for
    testing a combination shift
    register
        and counter */

    wire data, clk;
    // nets to connect up the pieces
    wire delayedData;
    // data out of the fifo
    wire [31:0] nOnes;
    // number of ones contained in
    fifo

        // Module instances
        shiftAndCount SandC
        (delayedData, nOnes, data, clk);
    // shift register
        clkGen #(10) cg (clk);
    // generate the clock
        testGenerator tg (data,
        delayedData, nOnes, clk);
    // create data, check result

endmodule

module shiftAndCount (bitOut,
count, dataIn, clk);
    parameter width = 8;
    output bitOut;

```

•

```

// data shifted out
    output [31:0] count;
// count of ones
    input dataIn, clk;
// inputs

    integer count;
// the counter
    reg bitOut;
// temporary
    reg [width-1:0] lastBits;
// shift register

    initial begin count = 0;
lastBits = 0; end

    always @(posedge clk) begin
        bitOut = lastBits[width-
1];
        lastBits = (lastBits<<1)
| dataIn;
        if (bitOut > dataIn)
            count = count - 1;
        else
            if (bitOut < dataIn)
                count = count + 1;
        end
endmodule

module clkGen (clk);
    parameter period = 2;
    output clk;
    reg clk;

    initial clk = 0;
// start off with 0
    always
// clock loop
        #(period/2) clk = ~clk;
endmodule

module testGenerator (dataBit,
delayedBit, count, clk);
    output dataBit;
    input delayedBit;
    input [31:0] count;
    input clk;
    reg dataBit;

    task emitBits; // helper
task to emit n bits
        input [7:0] bits, n;
// task inputs
        begin
            repeat (n) begin
// assume clk is at negedge
                dataBit =
bits[0]; // take just the low
order bit

```

```

        bits = bits >> 1;
        @(negedge clk) ;
        end
// leave at negative edge
    end
endtask

    task check;
        input bit;
        input [31:0] shouldBe;
        begin
            if (delayedBit !=
bit)
                $display($time, "
delayed bit is %b but should be
%b",


delayedBit, bit);
            if (count !=
shouldBe)
                $display($time, "
Count is %d but should be %d",


count, shouldBe);
            end
        endtask

    initial begin
// produce test data, check
results
        $monitor($time, " dataBit:
%b delayedBit: %b", dataBit,
delayedBit);
        emitBits(0, 1);
// take care of first cycle
        emitBits('b10010, 5);
        check(0, 2);
        emitBits('b101101, 6);
        check(0, 5);
        emitBits('b01, 2);
        check(1, 5);
        $stop;
    end
endmodule

```

### III. 4-bit adder (gate version)

 

 

```

module system;
    /* This is a test fixture for
    testing a combination shift
    register
        and counter */

    wire data, clk;
    // nets to connect up the pieces
    wire delayedData;
    // data out of the fifo
    wire [31:0] nOnes;
    // number of ones contained in
    fifo

    // Module instances
    shiftAndCount SandC
    (delayedData, nOnes, data, clk);
    // shift register
    clkGen #(10) cg (clk);
    // generate the clock
    testGenerator tg (data,
    delayedData, nOnes, clk);
    // create data, check result

endmodule

module shiftAndCount (bitOut,
count, dataIn, clk);
    parameter width = 8;
    output bitOut;
    // data shifted out
    output [31:0] count;
    // count of ones
    input dataIn, clk;
    // inputs

```

•

```

        integer count;
// the counter
        reg bitOut;
// temporary
        reg [width-1:0] lastBits;
// shift register

        initial begin count = 0;
lastBits = 0; end

        always @(posedge clk) begin
            bitOut = lastBits[width-
1];
            lastBits = (lastBits<<1)
| dataIn;
            if (bitOut > dataIn)
                count = count - 1;
            else
                if (bitOut < dataIn)
                    count = count + 1;
            end
endmodule

module clkGen (clk);
    parameter period = 2;
    output clk;
    reg clk;

    initial clk = 0;
// start off with 0
    always
// clock loop
        #(period/2) clk = ~clk;
endmodule

module testGenerator (dataBit,
delayedBit, count, clk);
    output dataBit;
    input delayedBit;
    input [31:0] count;
    input clk;
    reg dataBit;

    task emitBits; // helper
task to emit n bits
        input [7:0] bits, n;
// task inputs
        begin
            repeat (n) begin
// assume clk is at negedge
                dataBit =
bits[0]; // take just the low
order bit
                bits = bits >> 1;
                @(negedge clk) ;
            end
// leave at negative edge
        end
end

```

```

        endtask

        task check;
            input bit;
            input [31:0] shouldBe;
            begin
                if (delayedBit !=
bit)
                    $display($time, "
delayed bit is %b but should be
%b",
delayedBit, bit);
                if (count !=
shouldBe)
                    $display($time, "
Count is %d but should be %d",
count, shouldBe);
            end
        endtask

        initial begin
// produce test data, check
results
            $monitor($time, " dataBit:
%b delayedBit: %b", dataBit,
delayedBit);
            emitBits(0, 1);
// take care of first cycle
            emitBits('b10010, 5);
            check(0, 2);
            emitBits('b101101, 6);
            check(0, 5);
            emitBits('b01, 2);
            check(1, 5);
            $stop;
        end
    endmodule

```

## IV. Practice

1. Thực hiện mạch cộng 16 bits dựa vào module cộng 4 bits đã có.